

# Lab 2: The ID Pipeline Stage

George Suarez and Patrick Duggin

October 31, 2018

## 1 Introduction

The objective of this lab is to implement and test the Instruction Decode (ID) pipeline stage and integrate it with the IF stage. There are five modules to implement which are: I\_DECODE, CONTROL, REG, S\_EXTEND, and ID\_EX.

## 2 Interface

The CONTROL module receives the 6-bits of instruction code from the opcode field of IF\_ID\_instr and divides it into EX, M, and WB control lines.

Table 1: control Inputs

Name	Function
opcode	The 6-bits from the opcode field of IF_ID_instr

Table 2: control Outputs

Name	Function
EX	The 4-control bit
M	The 3-control bit
WB	The 2-control bit

The REGISTER module fills 32-bit registers/addresses with zero where a reg\_write control line specifies a 1 for writing data and a 0 for not writing data. This module outputs two 32-bit registers where one of them holds the contents for the source registers and the contents for the target registers.

Table 3: register Inputs

Name	Function
rs	The 5-bit source register
rt	The 5-bit target register
rd	The 5-bit destination register
write_data	The 32-bit data
reg_write	The 1-bit that toggles between 1 or 0

Table 4: register Outputs

Name	Function
A	The 32-bit register that holds the result of REG[rs]
B	The 32-bit register that holds the result of REG[rd]

The combinational module `S_EXTEND` extends a 16-bit number into a 32-bit number and controls if the number is a positive or negative.

Table 5: s\_extend Inputs

Name	Function
Next_end	The 16-bit immediate field of IF_ID_instr

Table 6: s\_extend Outputs

Name	Function
extend	The 32-bit sign-extended value

The `ID_EX` module is the pipeline register that inputs and outputs the program counter and instruction.

Table 7: id\_ex Inputs

Name	Function
ctlwb_out	The 2-control bit for write back (WB)
ctlm_out	The 3-control bit for memory (M)
ctlex_out	The 4-control bit for execute (EX)
npc	The 32-bit new program counter
readdata1	The 32-bit data from REG[rs]
readdata2	The 32-bit data from REG[rt]
signext_out	The 32-bit value from s_extend
instr_2016	The 5-bit instruction code from instr[20:16]

instr_1511	The 5-bit instruction code from instr[15:11]
------------	--


Table 8: id\_ex Outputs

Name	Function
wb_ctlout	The 2-bit register that holds the result from ctlwb_out
wb_ctlm	The 3-bit register that holds the result from ctm_out
wb_ctlex	The 4-bit register that holds the result from ctlex_out
regdst	The 1-bit register that holds the result of ctlex_out[3]
alusrc	The 1-bit register that holds the result of ctlex_out[0]
npcout	The 32-bit register that holds the result of npcout
rdata1out	The 32-bit register that holds the result of readdata1
rdata2out	The 32-bit register that holds the result of readdata2
s_extendout	The 32-bit register that holds the result of signext_out
instrout_2016	The 5-bit register that holds the result of instr_2016
instrout_1511	The 5-bit register that holds the result of instr_1511

### 3 Design


The design of the CONTROL module takes in a 6-bit opcode that outputs the control bits for WB, M, and EX.

Figure 1: Control design

 


The design of the REG module takes in a 5-bit source register, a 5-bit target register, a 5-bit destination register, and a 32-bit data register that holds the data. Then it outputs two 32-bit registers that holds the contents of the source and target registers respectively.

*Figure 2: REG design*

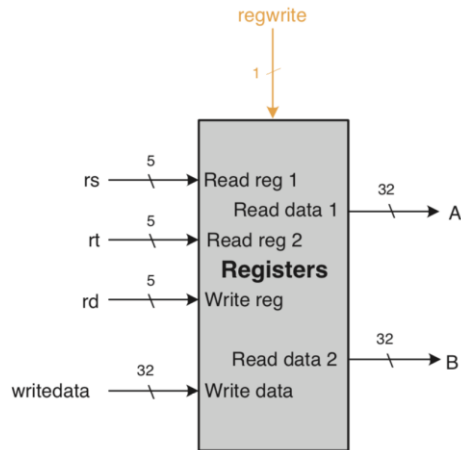

The design of the S\_EXTEND module takes in a 16-bit number and outputs the 32-bit version of that 16-bit number. Also maintains the characteristics of the number whether it is a positive or negative.


*Figure 3: S\_EXTEND design*

 

The design for the ID\_EX memory module has 9 control bits that is divided into 3 control wires that handles the write back, memory, and execution. It takes in a 32-bit NPC, two 32-bit read data registers, 32-bit sign extender, and two 5-bit instruction code

registers. Then it outputs the program counter and instructions.

*Figure 4: ID\_EX module design*

 

## 4 Implementation

*Listing 1: Implementation for control*

```
`timescale 1ns / 1ps

module control (
    input wire [5:0] opcode,
    output reg [3:0] EX,
    output reg [2:0] M,
    output reg [1:0] WB
);

parameter RTYPE = 6'b000000;
parameter LW = 6'b100011;
parameter SW = 6'b101011;
parameter BEQ = 6'b000100;
parameter NOP = 6'b100000;

initial begin
    /* Assign decimal representation of 0 to our output
       REG's here. Note the difference
```

```

*/
    EX <= 0;
    M <= 0;
    WB <= 0;
end

/* Assign the don't cares (X) to high impedance (Z)...
   For design correctness and more proper MIPS emulation
*/

always @ * begin
    case (opcode)
        RTYPE: begin
            EX <= 4'b1100; /* Note use of non-blocking operator
(<=) vs blocking operator (=) */
            M <= 3'b000;
            WB <= 2'b10;
        end
        /* Assign the remaining values according to the chart
in Lab Manuel.
        Either parametrize it, or hardcode at as is done for
RTYPE.
*/
        LW: begin
            EX <= 4'b0001;
            M <= 3'b010;
            WB <= 2'b11;
        end

        SW: begin
            EX <= 4'b0001;
            M <= 3'bz01;
            WB <= 2'b0z;
        end

        BEQ: begin
            EX <= 4'bz010;
            M <= 3'b100;
            WB <= 2'b0z;
        end

        NOP: begin
            EX <= 4'b0000;
            M <= 3'b000;
            WB <= 2'b00;
        end

        default: $display ("Opcode not recognized.");
    endcase
end
endmodule // control

```

*Listing 2: Implementation for register*

```
`timescale 1ns / 1ps

module register (
    input [4:0] rs,
    input [4:0] rt,
    input [4:0] rd,
    input [31:0] write_data,
    input reg_write,
    output reg [31:0] A,    // rs output
    output reg [31:0] B    // rd output
);

    // Register declaration
    reg [31:0] REG [0:31]; // Gives us 32 registers, each 32 bits
    long

    integer i;

    initial begin
        A <= 0;
        B <= 0;

        // Initialize our registers
        for (i = 0; i < 32; i = i + 1)
            REG[i] <= 0;

        // Display contents of the first 9 registers
        $display("From Register Memory:");
        for (i = 0; i < 9; i = i + 1)
            $display("\tREG[%0d] = %0d", i, REG[i]);

        // Display last register
        $display("\t...");
        $display("\tREG[%0d] = %0d", 31, REG[31]);
    end

    always @ * begin
        A <= REG[rs];
        B <= REG[rt];

        // Write data using index rd
        if (rd != 0 && reg_write)
            REG[rd] <= write_data;
    end

endmodule // register
```

*Listing 3: Implementation for s\_extend*

```
`timescale 1ns / 1ps

module s_extend(
    input wire [15:0] next_end,
    output reg [31:0] extend
);

    always @ * begin
        // Replicate signed bit 16 times then concatenate
        extend = { {16{next_end[15]}}, next_end };
    end

endmodule // s_extend
```

*Listing 4: Implementation for id\_ex*

```
`timescale 1ns / 1ps

module id_ex(
    input wire [1:0] ctlwb_out,
    input wire [2:0] ctlm_out,
    input wire [3:0] ctlex_out,
    input wire [31:0] npc, readdata1, readdata2, signext_out,
    input wire [4:0] instr_2016, instr_1511,
    output reg [1:0] wb_ctlout,
    output reg [2:0] m_ctlout,
    output reg regdst, alusrc,
    output reg [1:0] aluop,
    output reg [31:0] npcout, rdata1out, rdata2out,
    s_extendout,
    output reg [4:0] instrout_2016, instrout_1511
);

    initial begin
        // Assign 0's to everything
        wb_ctlout <= 0;
        m_ctlout <= 0;
        regdst <= 0;
        aluop <= 0;
        alusrc <= 0;
        npcout <= 0;
        rdata1out <= 0;
        rdata2out <= 0;
        s_extendout <= 0;
        instrout_2016 <= 0;
        instrout_1511 <= 0;
    end

    always @ * begin
        // Wire the inputs to the outputs corresponding outputs
        #1
    end
```



```

        wb_ctlout <= ctlwb_out;
        m_ctlout <= ctlm_out;
        regdst <= ctlex_out[3];
        aluop <= ctlex_out[2:1];
        alusrc <= ctlex_out[0];
        npcout <= npc;
        rdata1out <= readdata1;
        rdata2out <= readdata2;
        s_extendout <= signext_out;
        instrout_2016 <= instr_2016;
        instrout_1511 <= instr_1511;
    end
endmodule // id_ex

```

*Listing 5: Implementation for the top-level I\_DECODE module*

```

`timescale 1ns / 1ps

module I_DECODE(
    input wire [31:0] IF_ID_instrout,
    input wire [31:0] IF_ID_npcout,
    input wire [4:0] MEM_WB_rd,
    input wire MEM_WB_regwrite,
    input wire [31:0] WB_mux5_writedata,
    output wire [1:0] wb_ctlout,
    output wire [2:0] m_ctlout,
    output wire regdst, alusrc,
    output wire [1:0] aluop,
    output wire [31:0] npcout, rdata1out, rdata2out,
    s_extendout,
    output wire [4:0] instrout_2016, instrout_1511
);

    // Signals
    wire [3:0] ctlex_out;
    wire [2:0] ctlm_out;
    wire [1:0] ctlwb_out;
    wire [31:0] readdata1, readdata2, signext_out;

    // instantiations
    control control2(
        .opcode( IF_ID_instrout[31:26] ), // input
        .EX( ctlex_out ), // outputs
        .M( ctlm_out ),
        .WB( ctlwb_out )
    );

    register register2(
        .rs( IF_ID_instrout[25:21] ), // inputs
        .rt( IF_ID_instrout[20:16] ),
        .rd( MEM_WB_rd ),
        .writedata( WB_mux5_writedata ),

```

```

        .regwrite( MEM_WB_regwrite ),
        .A(readdata1),                //outputs
        .B(readdata2)
    );

    s_extend s_extend2(
        .nextend( IF_ID_instrout[15:0] ),
        .extend( signext_out )
    );

    id_ex id_ex2(
        .ctlwb_out( ctlwb_out ),    // 9 inputs
        .ctlm_out( ctm_out ),
        .ctllex_out( ctllex_out ),
        .npc( IF_ID_npcout ),
        .readdat1( readdata1 ),
        .readdat2( readdata2 ),
        .signext_out( signext_out ),
        .instr_2016( IF_ID_instrout[20:16] ),
        .instr_1511( IF_ID_instrout[15:11] ),
        .wb_ctlout( wb_ctlout ),    // outputs
        .m_ctlout( m_ctlout ),
        .regdst( regdst ),
        .alusrc( alusrc ),
        .aluop( aluop ),
        .npcout( npcout ),
        .rdatalout( rdatalout ),
        .rdata2out( rdata2out ),
        .s_extendout( s_extendout ),
        .instrout_2016( instrout_2016 ),
        .instrout_1511( instrout_1511 )
    );

endmodule // I_DECODE

```

## 5 TestBench Design

The CONTROL test bench is designed to display the 6-bit opcode from the instructions code register and output what control bits are being used from the given instructions. Some opcodes should not be recognized if the control bits do not match any of the instructions code (see Listing 6 for the Verilog code).

The REG test bench is designed to assign source, target, and destination registers with random data with toggling the reg\_write wire to either 1 for writing data or 0 for not writing data. Then the timing diagram will show a 5ns simulation that shows the contents of the registers (see Listing 7 for the Verilog code).

The S\_EXTEND test bench is designed to display two 16-bit numbers with one having 1 as the most significant bit and the other having 1 as the least significant bit. Then it displays the extended 32-bit version of those two numbers (see Listing 8 for the Verilog code).

*Listing 6: Control Test Bench*

```
module test ();  
    // Port wires  
    wire [08:0] controls;  
  
    // Register Declarations  
    reg [31:0] instr;  
  
    initial begin  
        instr[31:26] <= 6'b0;  
        $display("Time\t\tOPCODE\t\t\t\tControlbits\n");  
        $monitor("%0d\t\t\t%b\t\t%b ", $time, instr, controls);  
        #20; $finish;  
    end  
  
    always begin  
        #1 instr[31:26] = 35;  
        #1 instr[31:26] = 43;  
        #1 instr[31:26] = 4;  
        #1 instr[31:26] = 100;  
        #1 instr[31:26] = 0;  
    end  
  
    control controll1 ( instr[31:26], controls );  
endmodule
```

### *Listing 7: Register Test Bench*

```
`timescale 1ns / 1ps

module test;

    // Outputs
    wire [31:0] A, B;

    // Inputs
    reg [4:0] rs, rt, rd;
    reg [31:0] write_data;
    reg reg_write;

    register uut( .rs( rs ),
                  .rt( rt ),
                  .rd( rd ),
                  .write_data( write_data ),
                  .reg_write( reg_write ),
                  .A( A ),
                  .B( B ) );

    initial
    begin
        rs = 0;
        rt = 1;
        reg_write = 0;

        #1
        rs = 2;
        rt = 3;
        rd = 3;
        write_data = 100;

        #1
        rs = 4;
        rt = 5;
        reg_write = 1;

        #1
        reg_write = 0;
        rt = 3;

        #1
        rs = 6;
        reg_write = 1;
        rd = 6;
        write_data = 100;

        #1 $finish;
    end
endmodule
```

*Listing 8: Sign Extend Test Bench*

```
module test();
    // Port Wires
    wire [31:0] se_out;

    // Register Declarations
    reg [15:0] se_in;

    initial begin
        se_in = 0;
        #1 se_in = 16'b10;
        #1 se_in = 16'b01;
    end

    initial begin
        $monitor("Time = %0d\tse_in = %b\tse_out = %b", $time, se_in,
se_out);
    end

    s_extend s_extend1( .next_end( se_in ), .extend( se_out ) );
endmodule
```

## 6 Simulation

*Figure 5: Control test results from Listing 6*

Time	OPCODE	Controlbits
0	000000xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz1100
1	100011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
2	101011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
3	000100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
Opcode not recognized.		
4	100100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
5	000000xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz1100
6	100011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
7	101011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
8	000100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
Opcode not recognized.		
9	100100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
10	000000xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz1100
11	100011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
12	101011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
13	000100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
Opcode not recognized.		
14	100100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
15	000000xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz1100
16	100011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
17	101011xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz0001
18	000100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010
Opcode not recognized.		
19	100100xxxxxxxxxxxxxxxxxxxxxxxx	zzzzz010

Figure 6: Register Timing diagram from 0ns – 5ns

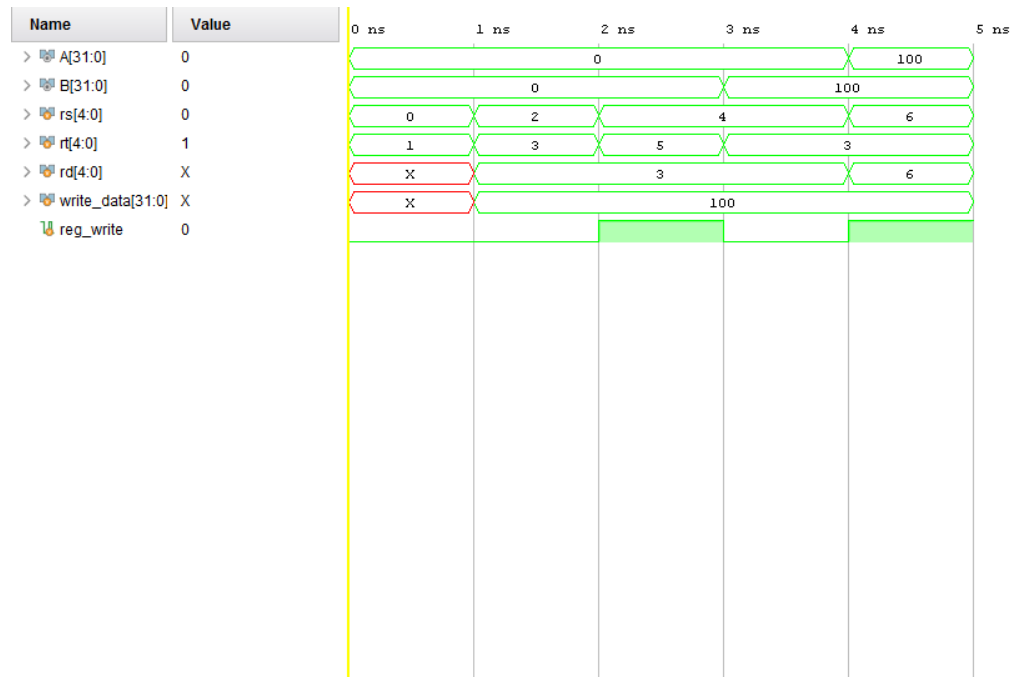


Figure 7: Sign extend test results from Listing 8

```

Time = 0   se_in = 0000000000000000   se_out = 00000000000000000000000000000000
Time = 1   se_in = 0000000000000010   se_out = 00000000000000000000000000000010
Time = 2   se_in = 0000000000000001   se_out = 00000000000000000000000000000001

```

## 7 Conclusions

The instruction decode stage for this lab was successfully implemented. The main thing we learned in doing this lab is how to run individual test benches in Vivado, and how to connect the instruction fetch stage with the instruction decode stage together. What we would have done differently in this lab is to implement a module, and then test that module before starting on the next module.