

Lab 1: The Instruction Fetch Stage

George Suarez

October 17, 2018

1 Introduction

The objective of this lab is to implement and test the Instruction Fetch (IF) pipeline stage of the MIPS five stage pipeline. There are five modules that need to be implemented which are: the program counter, the incrementer, the MUX, the memory, and the instruction fetch ID latch. All of these modules will make up the Instruction Fetch stage.

2 Interface

The program counter module takes in a 32-bit number that represents the New Program Counter (NPC), updates the current PC to the NPC value, and outputs a 32-bit number to the rest of the dependent modules.

Table 1: pc_mod Inputs

Name	Function
npc	The current 32-bit PC value

Table 2: pc_mod Outputs

Name	Function
pc_out	The updated 32-bit PC value

The incrementer module takes in a 32-bit constant 1 and a 32-bit PC value. Then the two inputs are added together, and outputs the result to another 32-bit wire.

Table 3: incrementer Inputs

Name	Function
pc_in	The 32-bit number that is the current PC

	value
--	-------

Table 4: incrementer Outputs

Name	Function
pc_out	The updated 32-bit number that is the result of incrementing pc_in by 1.

The MUX module takes in the next sequential PC value and the PC value that is calculated in the Execute stage depending on the value of the select line set in the Memory stage.

Table 5: mux Inputs

Name	Function
a	The 32-bit number that holds the next sequential PC value
b	The 32-bit number that holds the PC value that is calculated in the Execute stage
sel	The line that determines if inputs a or b will be selected to be the output

Table 6: mux Onputs

Name	Function
y	The 32-bit wire that holds the value that is specified via the select line

The instruction memory module takes in the current 32-bit PC value as its input and outputs the 32-bit instruction which that PC value is currently pointing at.

Table 7: mem Inputs

Name	Function
addr	The current 32-bit PC value

Table 8: mem Outputs

Name	Function
data	The 32-bit register which the PC value is currently pointing at

The Instruction Fetch-Decode latch (IF_ID_Latch) module takes in the next sequential PC value and address and outputs them to the next stage.

Table 9: IF_ID Inputs

Name	Function
instruction_in	The 32-bit wire from the Fetch stage
npc_in	The 32-bit wire from the Fetch stage

Table 10: IF_ID outputs

Name	Function
instruction_out	The updated 32-bit PC value from instruction_in
npc_out	The updated 32-bit PC value from npc_in

The Instruction Fetch module for the Instruction Fetch stage is where all the individual modules are connected to each other. It takes in a PC value and the sequential PC value, and outputs the IF_ID latch instructions and IF_ID latch PC value.

Table 11: ifetch Inputs

Name	Function
EX_MEM_PCSrc	The PC value from the instruction fetch-decode latch stage
EX_MEM_NPC	The 32-bit sequential PC value from the instruction fetch-decode latch stage


Table 12: ifetch Outputs

Name	Function
IF_ID_INSTR	The instructions from the instruction fetch-decode latch stage
IF_ID_NPC	The PC value from the instructions fetch-decode latch stage

3 Design


The design of the program counter takes in a 32-bit New Program Counter (NPC), updates the current PC value to the NPC value, and outputs the results to all the dependent modules.

Figure 1: Program Counter design

 


The design of the incrementer takes in the current PC value and outputs the PC value incremented by 1.

Figure 2: Incrementer design

 


The design of the MUX module takes in a s0 and s1 wire in which a select line determines the next PC value depending if the line goes high (1) or low (1).

Figure 3: MUX design

 

The design for the instruction memory module takes in a 32-bit PC value, and outputs the 32-bit instruction depending on where the PC value is currently pointing at.

Figure 4: Memory module design

 

4 Implementation

Listing 1: Implementation for pc_mod

```
`timescale 1ns / 1ps

module pc_mod( output reg [31:0] pc_out, input wire [31:0] npc
);

    initial
    begin
        pc_out <= 0;
    end

    always @ ( npc )
    begin
        #1 pc_out <= npc;
    end

endmodule
```

Listing 2: Implementation for incrementer

```
`timescale 1ns / 1ps

module incrementer ( input wire [31:0] pc_in, output wire
[31:0] pc_out );

    assign pc_out = pc_in + 1; // Increment PC by 1

endmodule
```

Listing 3: Implementation for mem

```
module mem(
    output reg [31:0] data,
    input wire [31:0] addr
);

    // Register Declarations
    reg [31:0] MEM[0:127];

    // Initialize Registers
    initial begin
        MEM[0] <= 'hA00000AA;
        MEM[1] <= 'h10000011;
        MEM[2] <= 'h20000022;
        MEM[3] <= 'h30000033;
        MEM[4] <= 'h40000044;
        MEM[5] <= 'h50000055;
        MEM[6] <= 'h60000066;
        MEM[7] <= 'h70000077;
        MEM[8] <= 'h80000088;
        MEM[9] <= 'h90000099;
    end

    always @ ( addr )
    begin
        data <= MEM[addr];
    end
endmodule
```

Listing 4: Implementation for if_id module

```
`timescale 1ns / 1ps

module if_id ( output reg [31:0] instructions_out, npc_out,
               input wire [31:0] instructions_in, npc_in
               );

    initial begin
        instructions_out <= 0;
        npc_out <= 0;
    end

    always @ * begin
        #1
        instructions_out <= instructions_in;
        npc_out <= npc_in;
    end
endmodule
```

Listing 5: Implementation for the top-level Instruction Fetch module

```
module I_FETCH (
    input EX_MEM_PCSrc,
    input wire [31:0] EX_MEM_NPC,
    output wire [31:0] IF_ID_INSTR, IF_ID_NPC
);

    // signals
    wire [31:0] PC;
    wire [31:0] data_out;
    wire [31:0] npc, npc_mux;

    // instantiations
    mux mux1 ( .y(npc_mux),
               .a(EX_MEM_NPC),
               .b(npc),
               .sel(EX_MEM_PCSrc));

    pc_mod pc_mod1 ( .pc_out(PC),
                     .npc(npc_mux));

    mem mem1 ( .data(data_out),
               .addr(PC));

    if_id if_id1 ( .instructions_out(IF_ID_INSTR),
                   .npc_out(IF_ID_NPC),
                   .instructions_in(data_out),
                   .npc_in(npc));

    incrementer incrementer1 ( .pc_out(npc),
                               .pc_in(PC));

endmodule
```

5 Test Bench Design

This test bench is designed to simulate instruction fetch routines over a *20ns* simulated run. The PC value starts at 0 initially and jumps to 1 after 9 cycles, and then jumps the PC value to 5 in which it outputs all the instruction fetch routines that were in the instruction memory module (Listing 3).

Listing 6: Instruction Fetch Test Bench

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
```

```

// Engineer:
//
// Create Date: 10/17/2018 12:15:19 PM
// Design Name:
// Module Name: pipeline
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
////////////////////////////////////

module pipeline();

    // Inputs
    reg EX_MEM_PCSrc;
    reg [31:0] EX_MEM_NPC;

    // Outputs
    wire [31:0] IF_ID_INSTR;
    wire [31:0] IF_ID_NPC;

    // Instantiate the Unit Under Test (UUT)
    I_FETCH uut (
        .EX_MEM_PCSrc(EX_MEM_PCSrc),
        .EX_MEM_NPC(EX_MEM_NPC),
        .IF_ID_INSTR(IF_ID_INSTR),
        .IF_ID_NPC(IF_ID_NPC)
    );


    initial
    begin
        EX_MEM_NPC = 0;
        EX_MEM_PCSrc = 0;
        #9
        EX_MEM_PCSrc = 1;
        EX_MEM_NPC = 5;
        #1
        EX_MEM_PCSrc = 0;
        #10;
        $stop;
    end

endmodule

```



6 Simulation

Figure 5: Timing diagram from 0ns – 8ns

  

10.000 ns								
9 ns	10 ns	11 ns	12 ns	13 ns	14 ns	15 ns	16 ns	17 ns
00000005								
80000088	90000099	50000055	60000066	70000077	80000088	90000099	XXXXXXXX	
00000009	0000000a	00000006	00000007	00000008	00000009	0000000a	0000000b	0000000c

Figure 7: Timing diagram from 13ns – 20ns



7 Conclusions

The instruction fetch stage for this lab was successfully implemented. The main thing I learned in doing is how the instruction fetch-decode latch is designed and implemented in Verilog code. I never thought about using a top-level module that connects all the modules together into one since I just instantiate all the modules in the test bench. What I would do differently in this lab was to get more familiar with the Vivado software beforehand to save myself time to figure out how to add source files and debug the Verilog code.